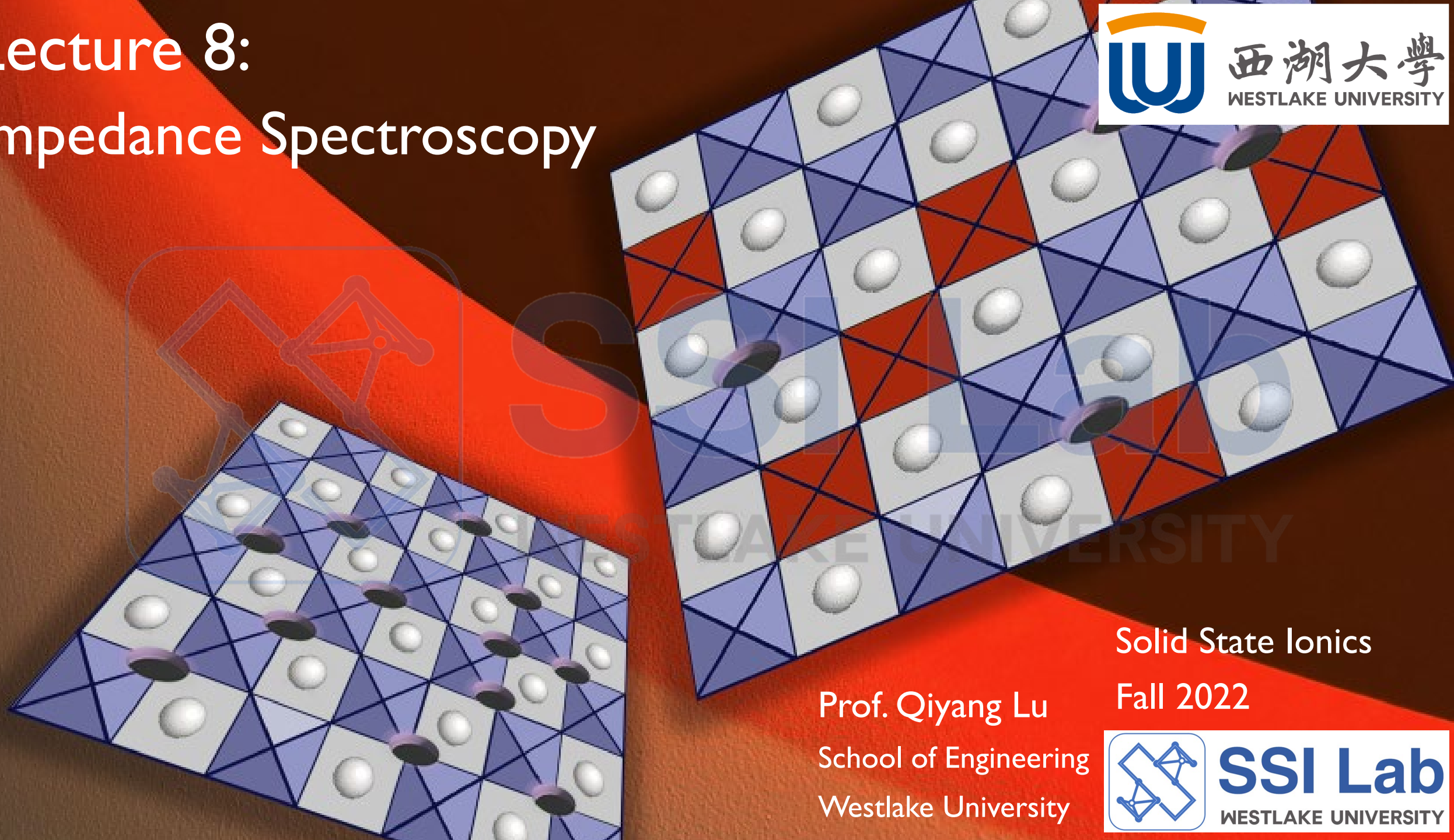


Lecture 8:

Impedance Spectroscopy



Solid State Ionics

Fall 2022

Prof. Qiyang Lu

School of Engineering

Westlake University





SSI Lab
WESTLAKE UNIVERSITY

Implications on the conductivity: series layer model


$$\sigma_{ion} = c_{V_O^{\bullet\bullet}} z_{V_O^{\bullet\bullet}} F M_{V_O^{\bullet\bullet}}$$

If we assume the mobility of $V_O^{\bullet\bullet}$ is the same in the bulk and grain boundary, then the ionic conductivity is mainly affected by the depletion of oxygen vacancies.


Consider the series layer model:

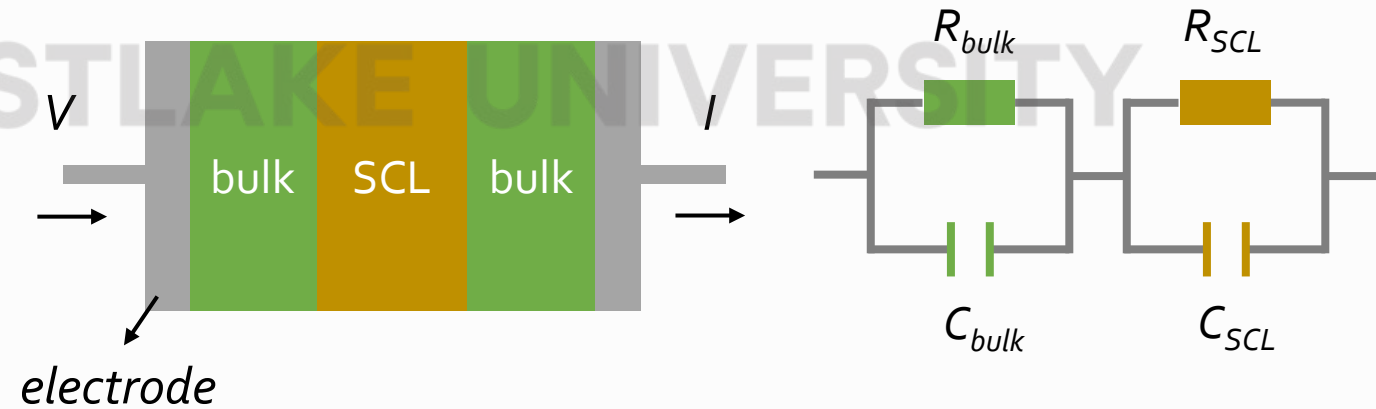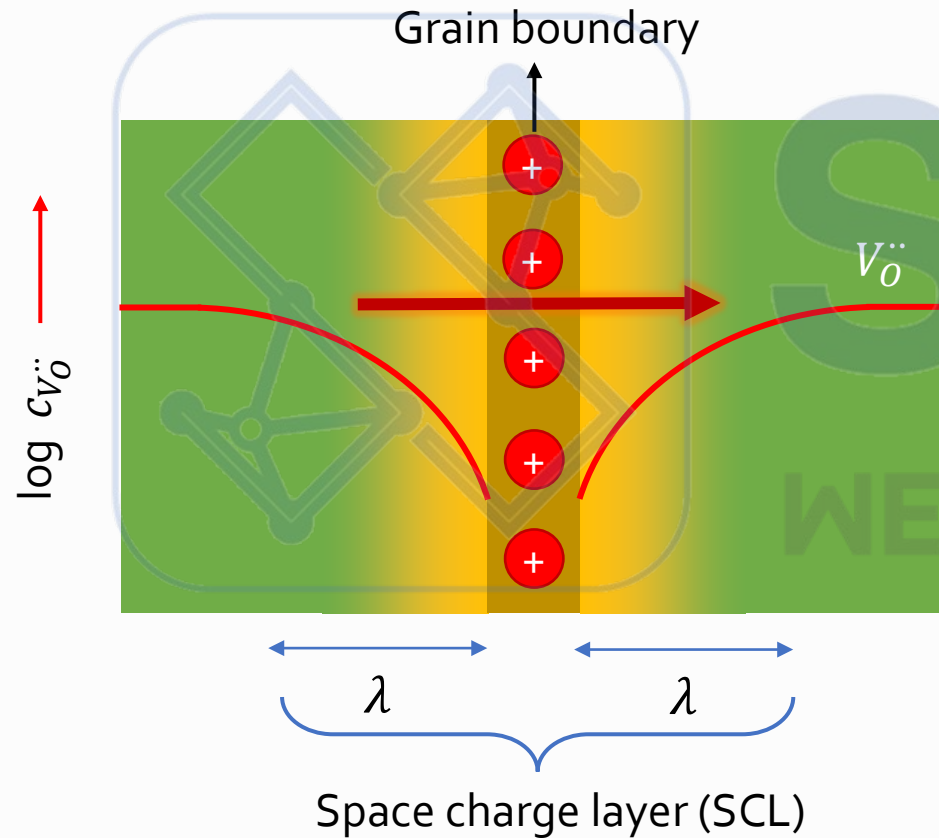
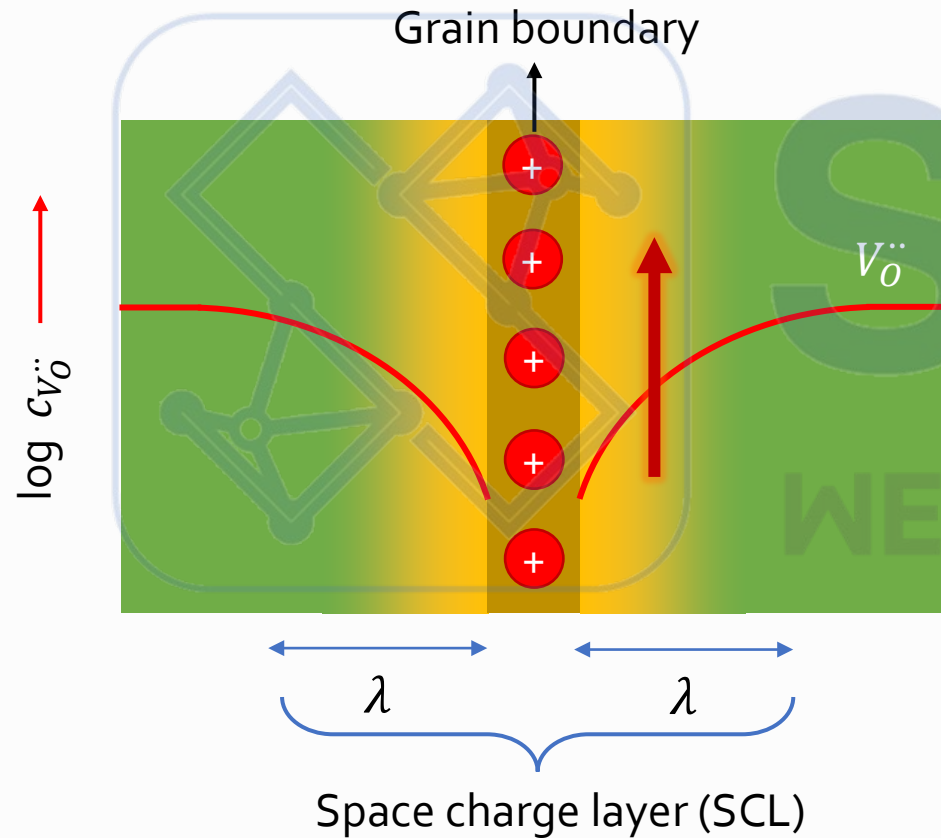
$$\sigma_{ion} = c_{V_O^{\bullet\bullet}} z_{V_O^{\bullet\bullet}} F M_{V_O^{\bullet\bullet}}$$




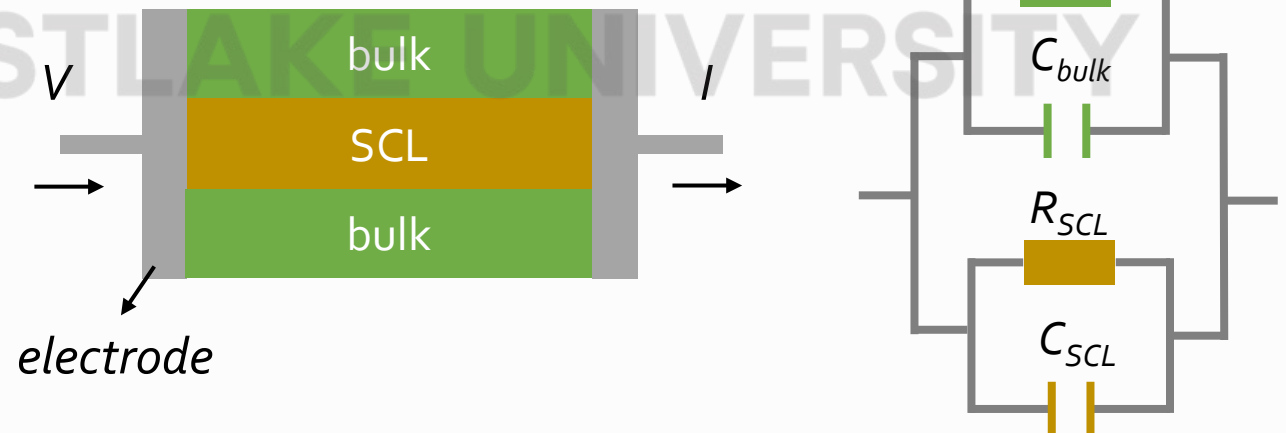We can also construct the parallel layer model:




How to evaluate resistance and capacitance?

Series layer model

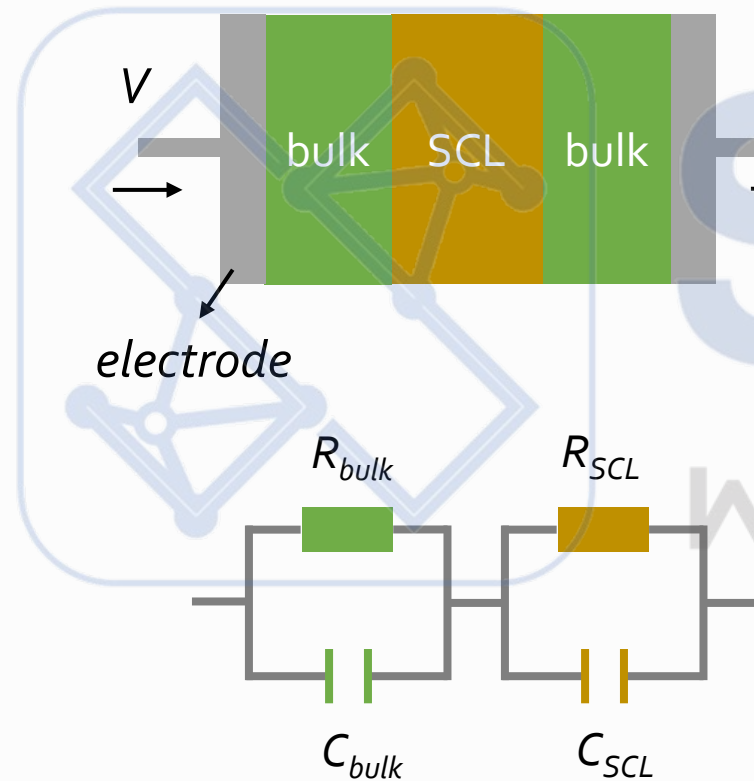

Parallel layer model

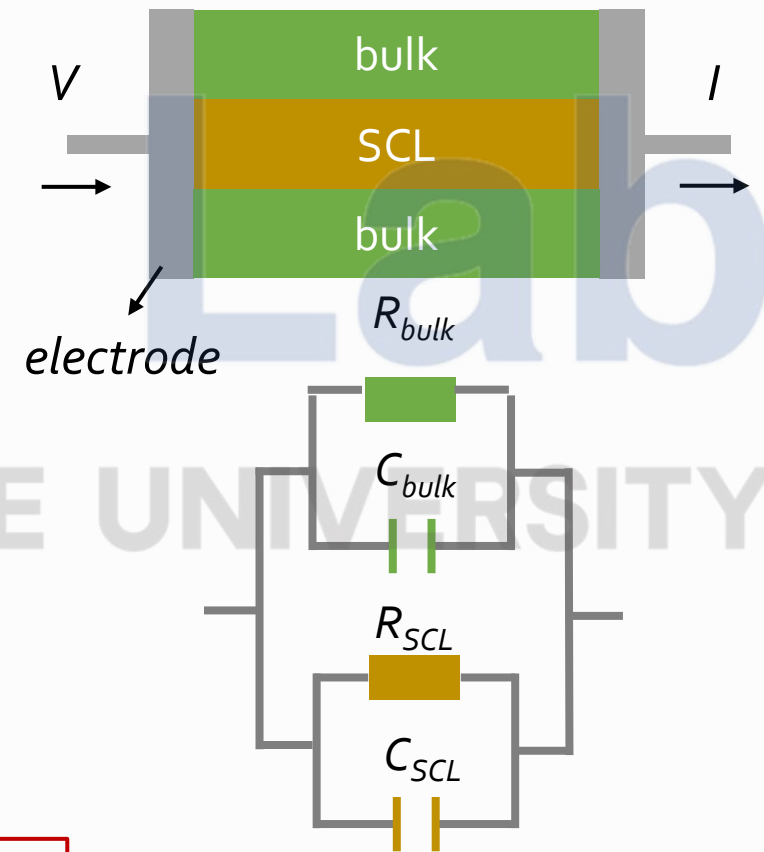




How to theoretically model and experimentally measure R_{SCL} & C_{SCL} ?

Electrochemical Impedance Spectroscopy (EIS):


- Why do we need electrochemical impedance spectroscopy? What problem are we trying to solve with this technique?
- How to understand the equivalent circuit model? How does the equivalent circuit model for a polycrystalline sample with grain boundaries look like?

Goal of this lecture: you should be able to answer the questions above by the end of this lecture :)

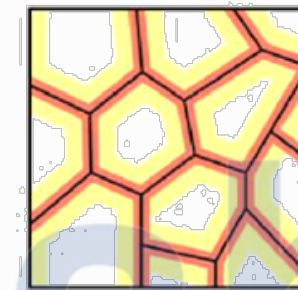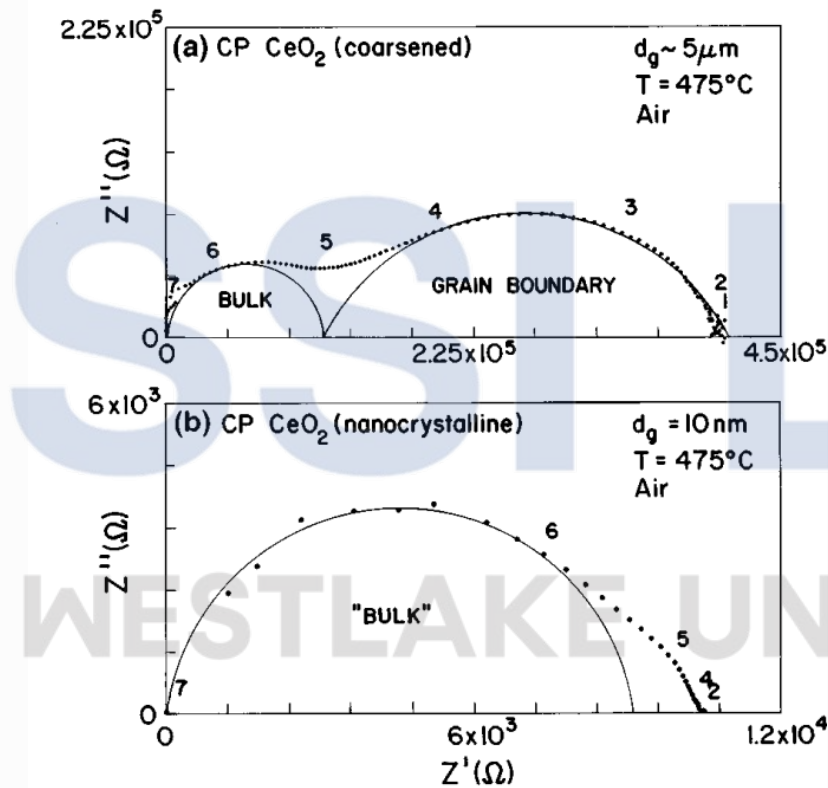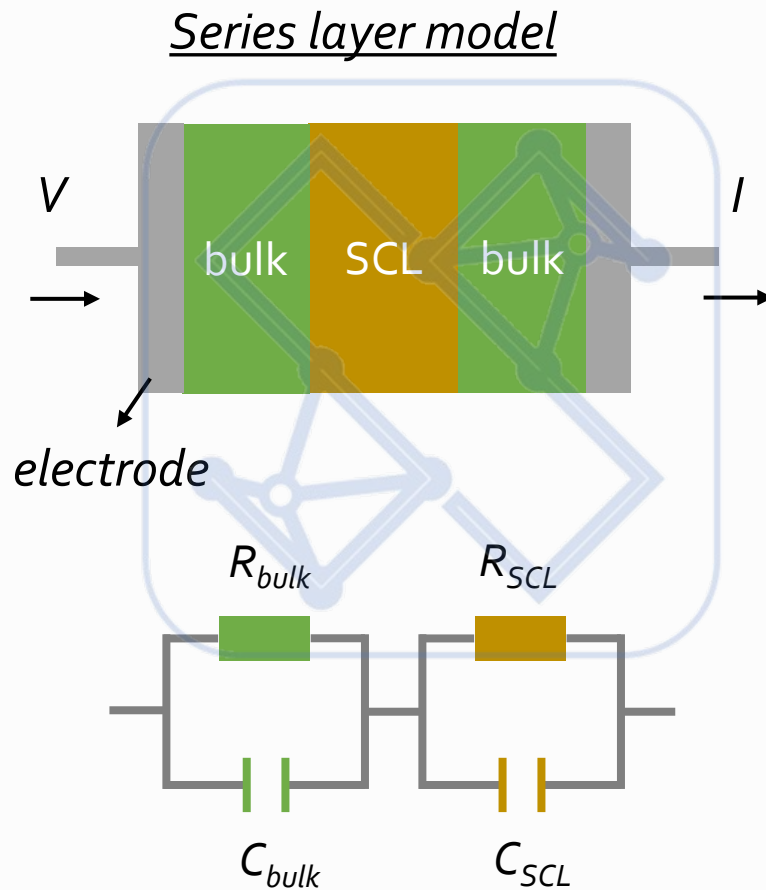Why do we need Electrochemical Impedance Spectroscopy?



Coarse-grained

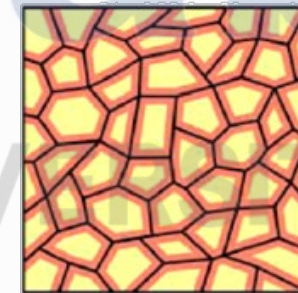


Nanocrystalline


Time constant $\tau = RC \rightarrow$ separate the contribution of bulk and SCL in the **frequency domain** ($f = 1/\tau$).

The working principle of EIS

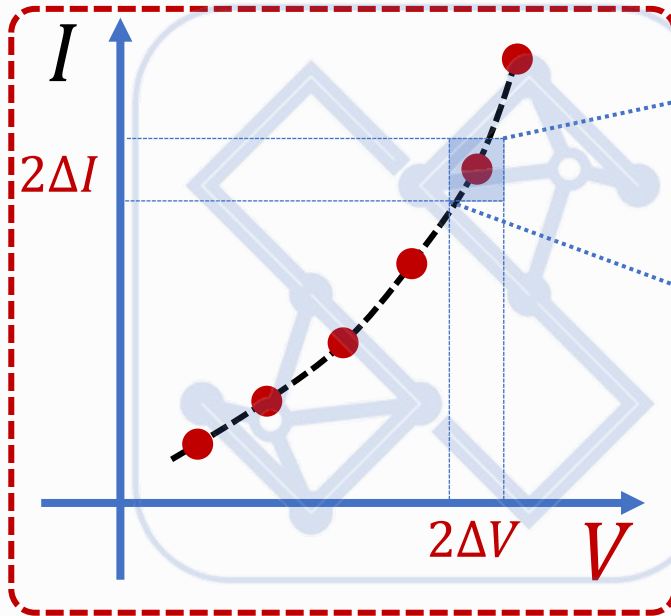I - V characteristics of an electrochemical system



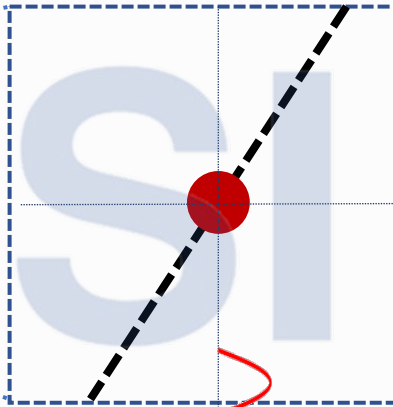Assumption: if the perturbation is small, then the I - V curve can be *linearized*.




$$I(t) = \Delta I \cos(\omega t - \varphi)$$

$$Z(\omega) = \frac{V(t)}{I(t)} = \frac{\Delta V}{\Delta I} \frac{\cos(\omega t)}{\cos(\omega t - \varphi)}$$


$$V(t) = \Delta V \cos(\omega t)$$


The working principle of EIS

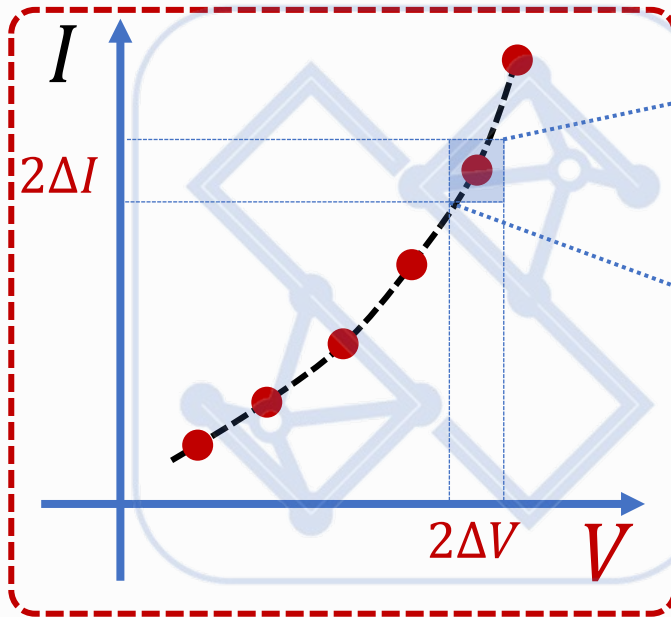I - V characteristics of an electrochemical system



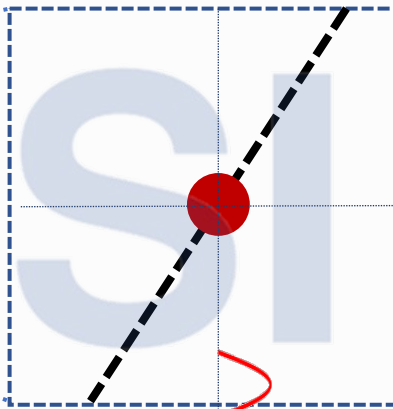Assumption: if the perturbation is small, then the I - V curve can be *linearized*.



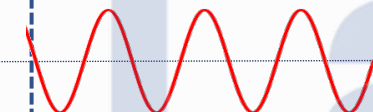


$$I(t) = \Delta I e^{i(\omega t - \varphi)}$$

Note: $i = \sqrt{-1}$

It is easier to use the complex form of waves, we have:

$$Z(\omega) = \frac{V(t)}{I(t)} = \frac{\Delta V}{\Delta I} \frac{e^{i\omega t}}{e^{i(\omega t - \varphi)}}$$

$$Z(\omega) = \underbrace{|Z| \cos \varphi}_{Z' \text{ or } \text{Re}(Z)} + i \underbrace{|Z| \sin \varphi}_{Z'' \text{ or } \text{Im}(Z)}$$

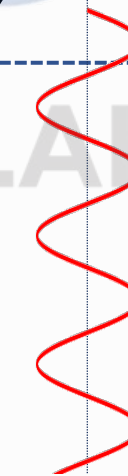

$$V(t) = \Delta V e^{i\omega t}$$


The working principle of EIS: Nyquist plot

$$Z(\omega) = |Z| \cos \varphi + i|Z| \sin \varphi$$

Z' or $Re(Z)$

Z'' or $Im(Z)$

$$Z(\omega) = Z' + iZ''$$

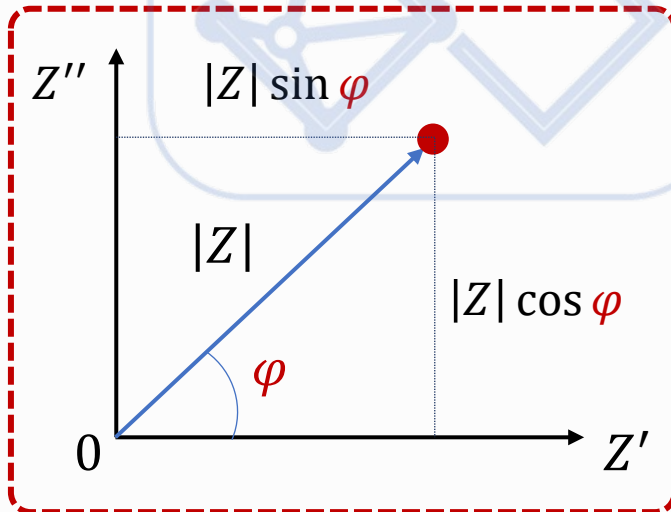

Nyquist plot
($Z' \sim Z''$ plot)

Note: more commonly
we plot $Z' \sim -Z''$

For a resistor, since I and V should always be *in phase*,
we have:



$$Z(\omega) = R$$

Note: only has the real part; invariant w/ frequency ω

For a capacitor, I and V should always be completely
out of phase



$$Z(\omega) = ?$$

$$I(t) = \Delta I e^{i(\omega t - \varphi)}$$

$$I(t) = \frac{dQ(t)}{dt}$$

$$Q(t) = \frac{\Delta I}{i\omega} e^{i(\omega t - \varphi)}$$


The working principle of EIS: Nyquist plot

For a capacitor, I and V should always be completely *out of phase*


$$\left. \begin{aligned} I(t) &= \Delta I e^{i(\omega t - \varphi)} \\ I(t) &= \frac{dQ(t)}{dt} \end{aligned} \right\} Q(t) = \frac{\Delta I}{i\omega} e^{i(\omega t - \varphi)}$$

$$V(t) = \frac{Q(t)}{C} = \frac{\Delta I}{i\omega C} e^{i(\omega t - \varphi)} = \frac{I(t)}{i\omega C}$$
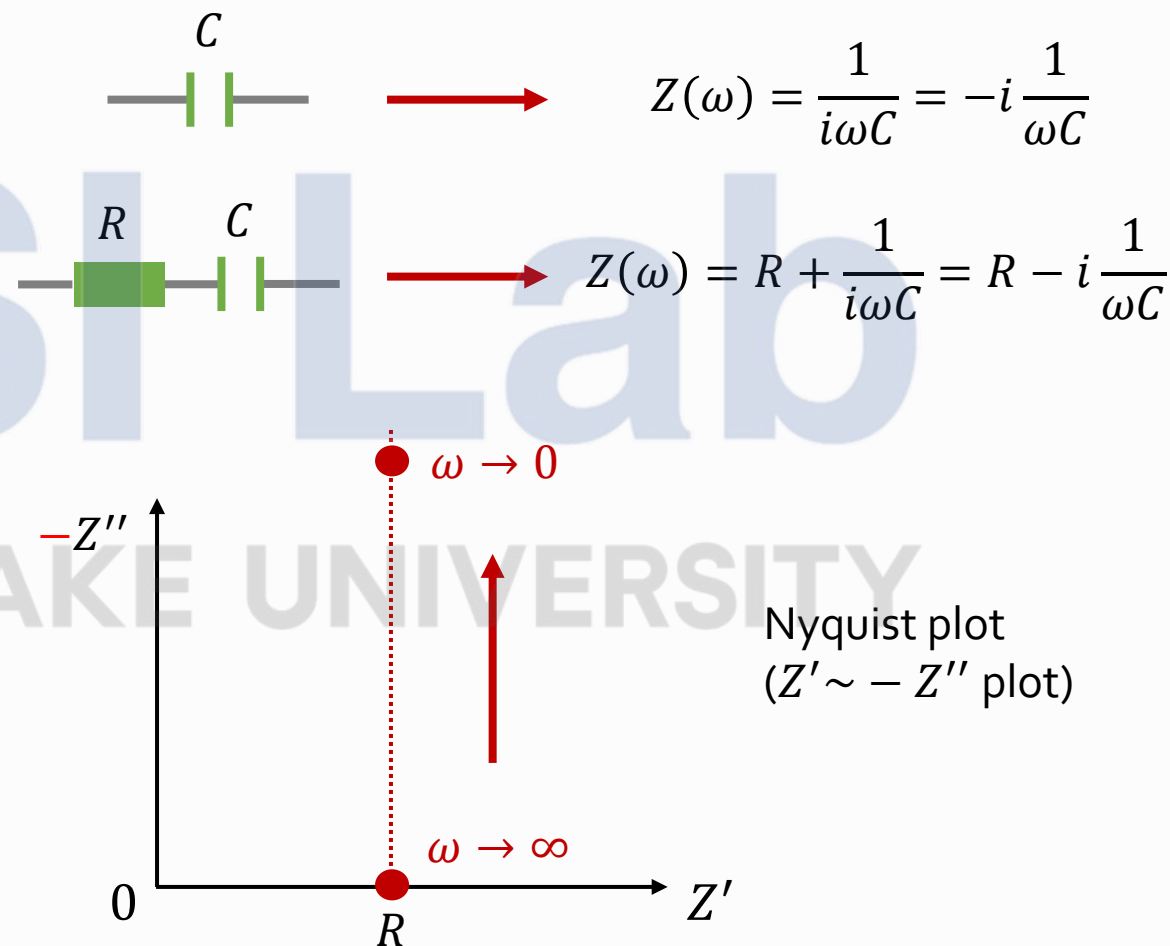
$$Z(\omega) = \frac{V(t)}{I(t)} = \frac{1}{i\omega C}$$




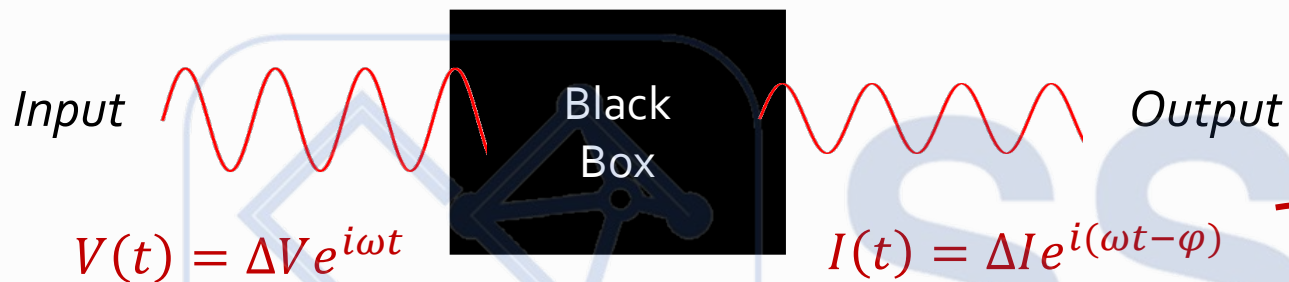
Which equivalent circuit should be chosen?




Note:

- The electrochemical system is a black box, *i.e.*, there is no prior knowledge on which circuit model should be used;
- There might be more than one equivalent circuit that can fit the data equally well.

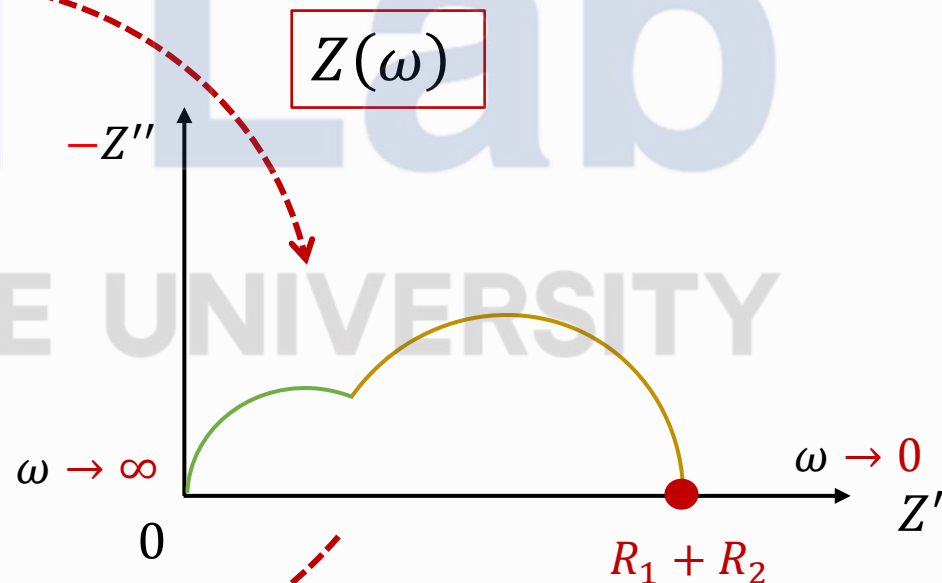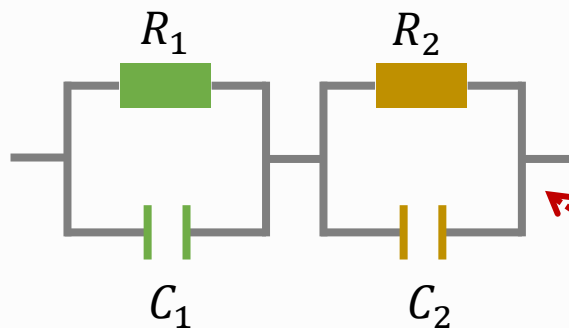Fit the impedance data with equivalent circuit




Nyquist plot: R-C in series

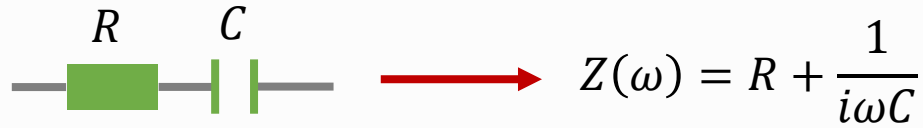

$$Z(\omega) = R \left(1 + \frac{1}{i\omega RC} \right)$$

We can define dimensionless impedance $\tilde{Z} = Z/R$
dimensionless frequency $\tilde{\omega} = \omega RC$

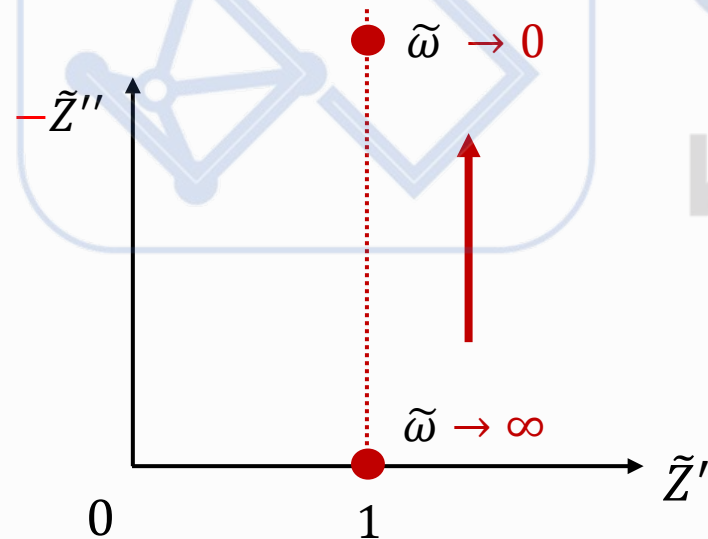
$$\tilde{Z}(\omega) = 1 + \frac{1}{i\tilde{\omega}}$$



Note: the advantages of using normalized dimensionless quantities are:

- The equations are much easier to write :)
- We can see how each physical quantity scales, e.g.
 - $\tilde{Z} = Z/R \rightarrow Z$ scales with resistance R ;
 - $\tilde{\omega} = \omega RC \rightarrow \omega$ scales inversely with RC . Keep in mind that time constant $\tau = RC$

Nyquist plot: R-C in parallel

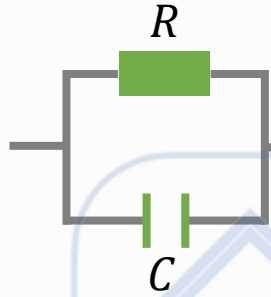

$$\tilde{Z}(\omega) = \frac{1}{1 + i\tilde{\omega}}$$


$$\tilde{Z}(\omega) = \frac{1}{1 + i\tilde{\omega}} = \frac{1}{1 + \tilde{\omega}^2} - \frac{i\tilde{\omega}}{1 + \tilde{\omega}^2}$$

$$\begin{aligned} \tilde{Z}' &= \frac{1}{1 + \tilde{\omega}^2} \\ -\tilde{Z}'' &= \frac{\tilde{\omega}}{1 + \tilde{\omega}^2} \end{aligned}$$


$$\left(\tilde{Z}' - \frac{1}{2}\right)^2 + (-\tilde{Z}'')^2 = \left(\frac{1}{2}\right)^2$$

It is a semi-circle ($\tilde{\omega} > 0$):



- Radius = 1/2
- Center = (1/2, 0)

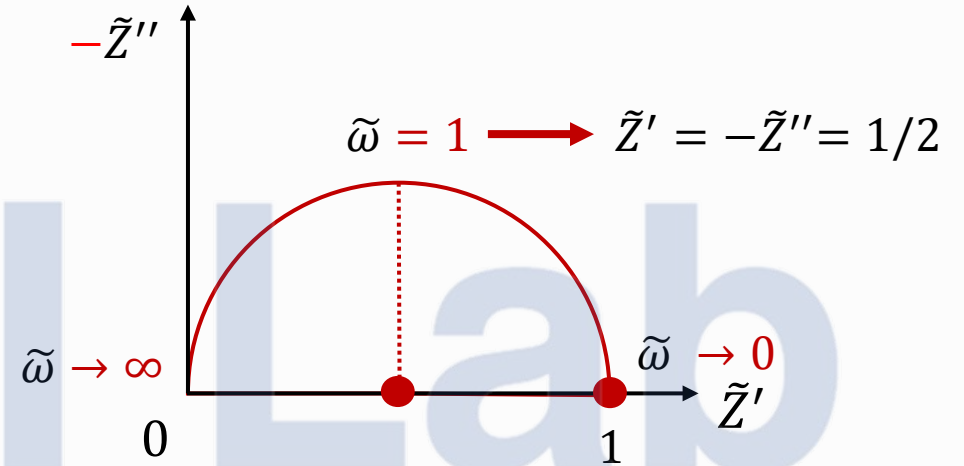


add dimensions

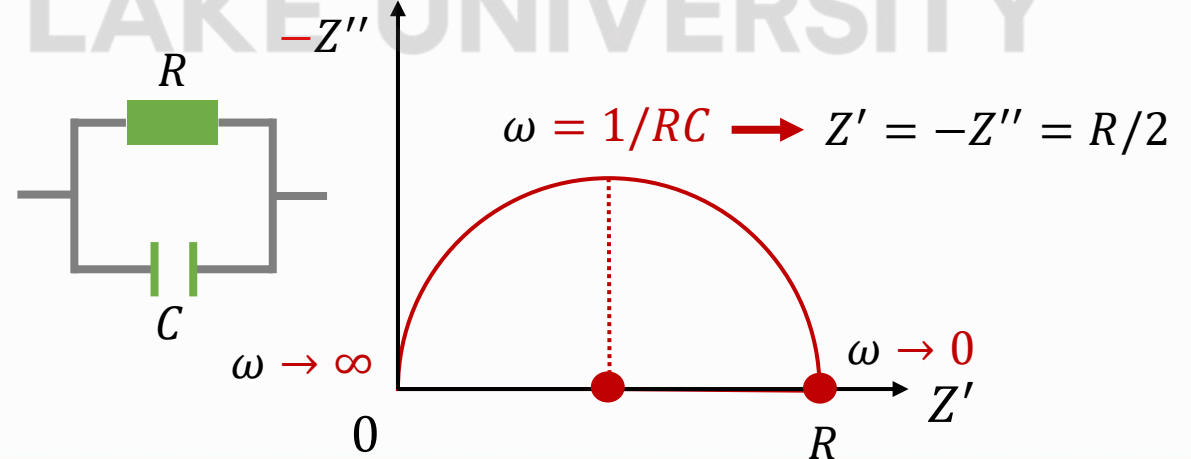

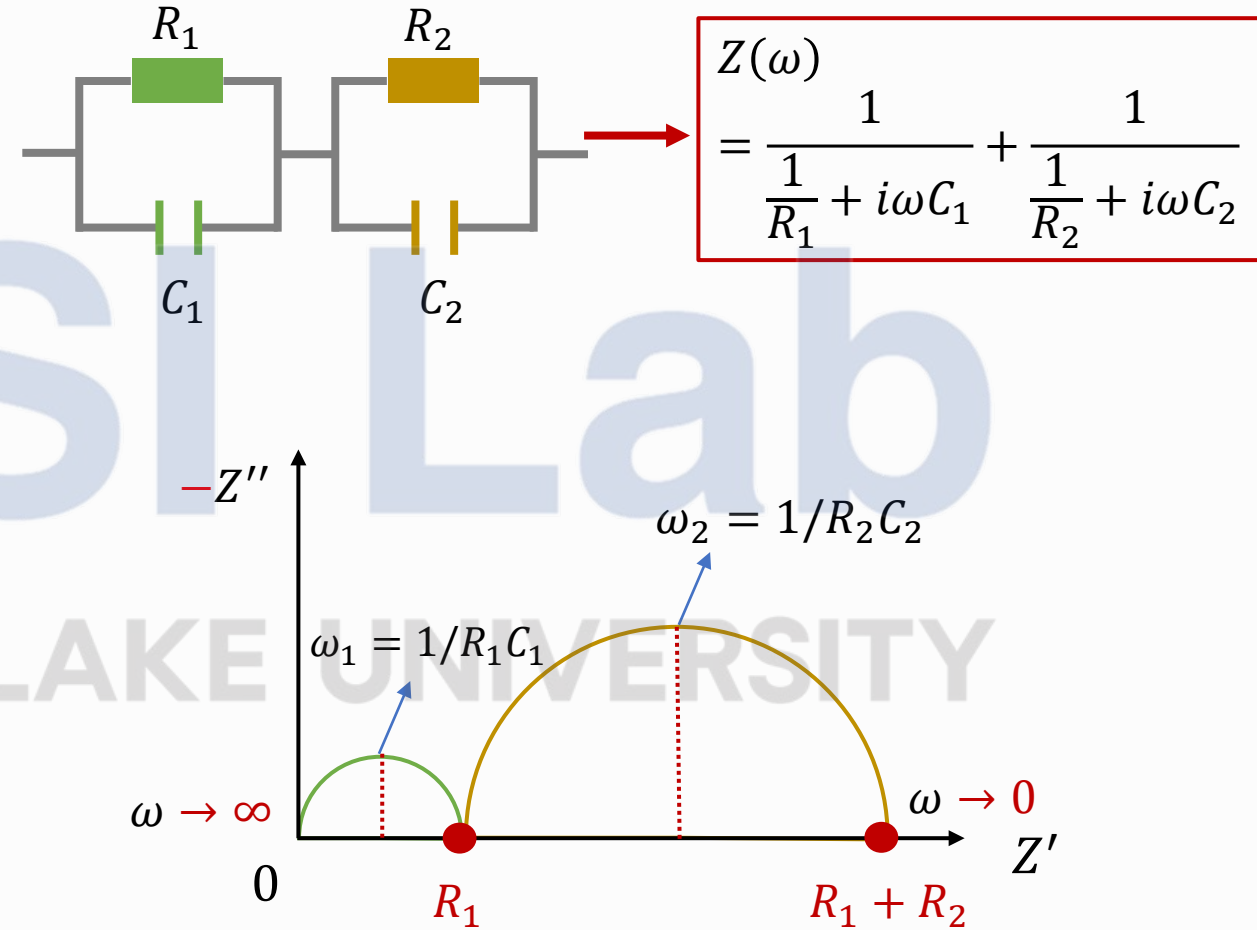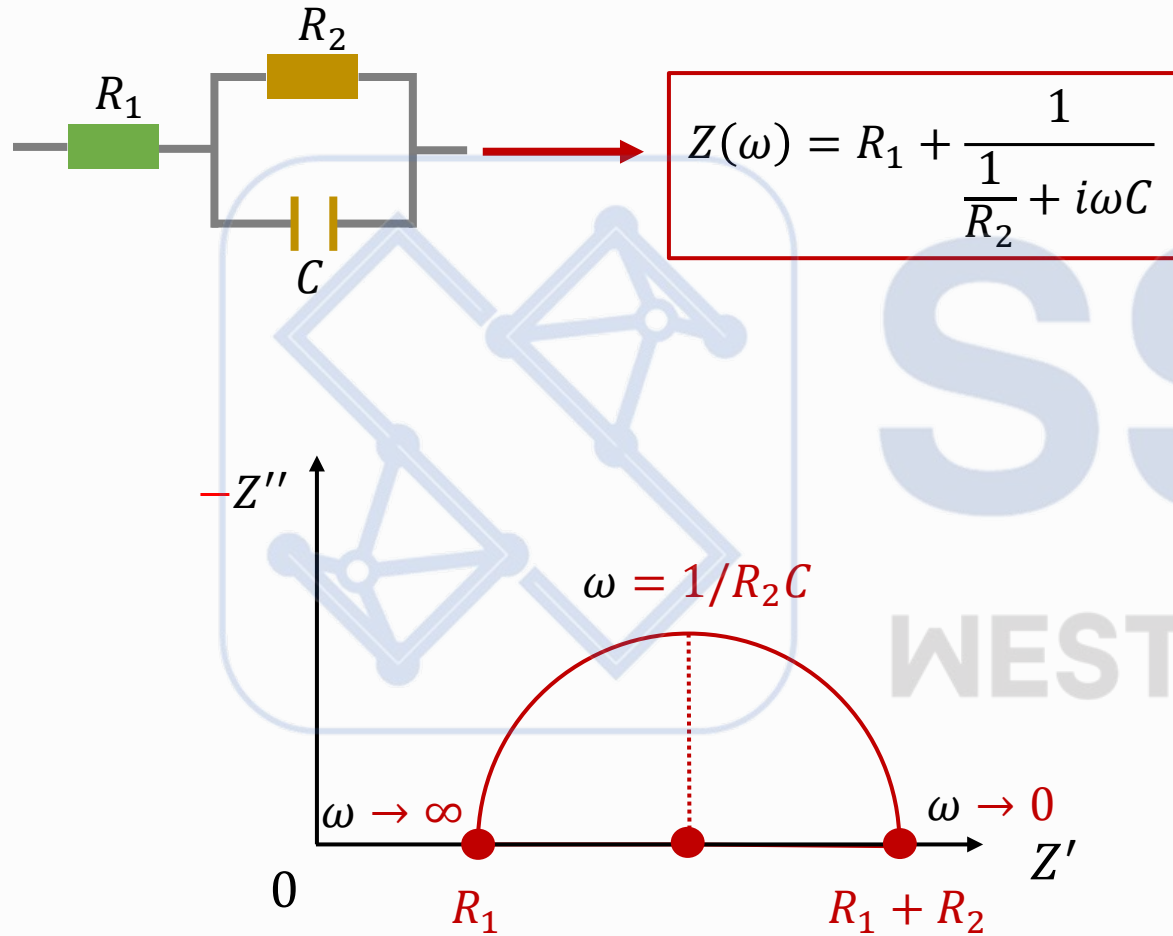
Nyquist plot: *more complicated circuits*



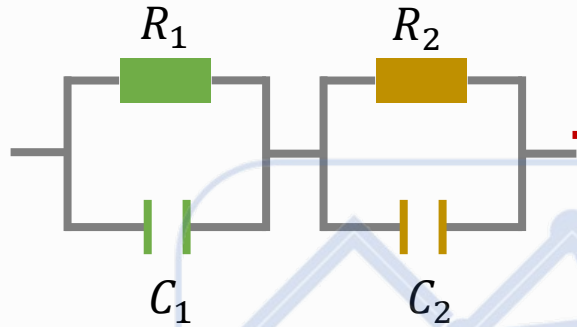
Nyquist plot: *more complicated circuits*


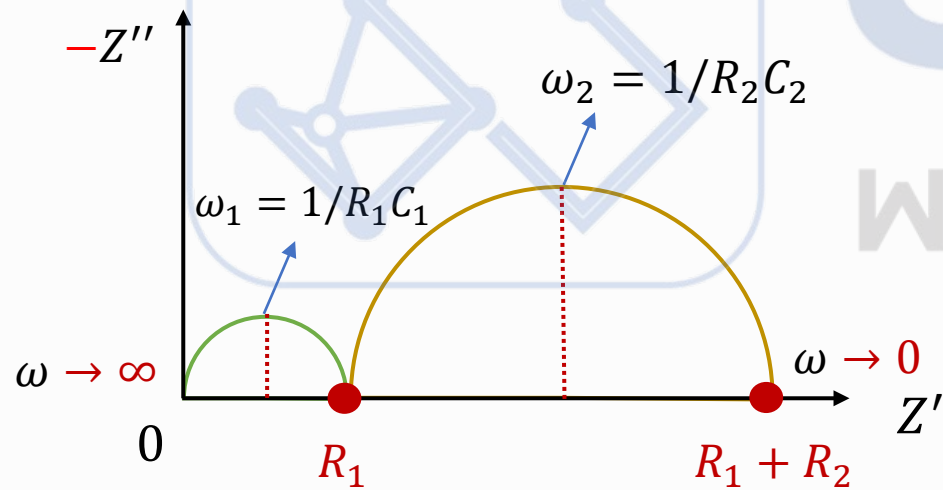
$$Z(\omega) = \frac{1}{\frac{1}{R_1} + i\omega C_1} + \frac{1}{\frac{1}{R_2} + i\omega C_2}$$




If ω_1 and ω_2
become closer

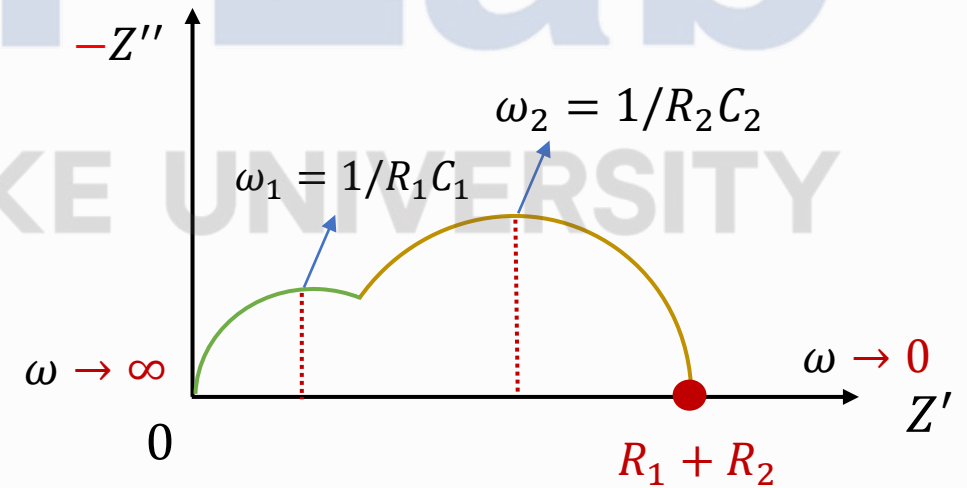

Brick layer model

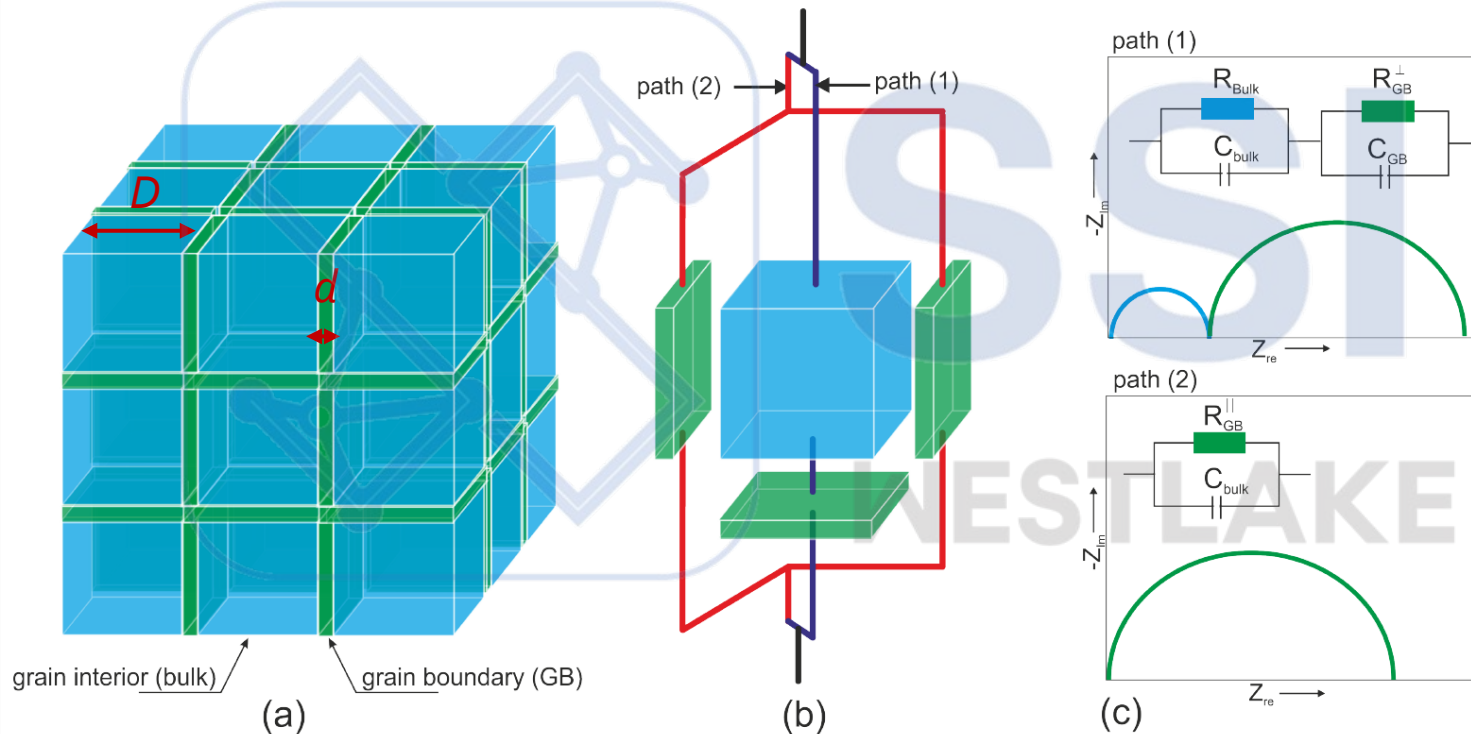Consider a polycrystalline material with much lower conductivity at the grain boundaries (GB) compared to the bulk



$$\frac{R_{bulk}}{R_{GB}} = \frac{\sigma_{GB}}{\sigma_{bulk}} \frac{D}{d}$$


($d \ll D$)

$$\frac{C_{bulk}}{C_{GB}} = \frac{\epsilon_{bulk}}{\epsilon_{GB}} \frac{d}{D}$$

- If $\sigma_{GB} \ll \sigma_{bulk}$, then path (1) (i.e., **series layer model**) will be dominate;
- If $\sigma_{GB} \gg \sigma_{bulk}$, then path (2) (i.e., **conducting along GBs**) might be activated.

PhD Thesis, Kiran Adepli, Max-Planck Institute for Solid State Research (2013)

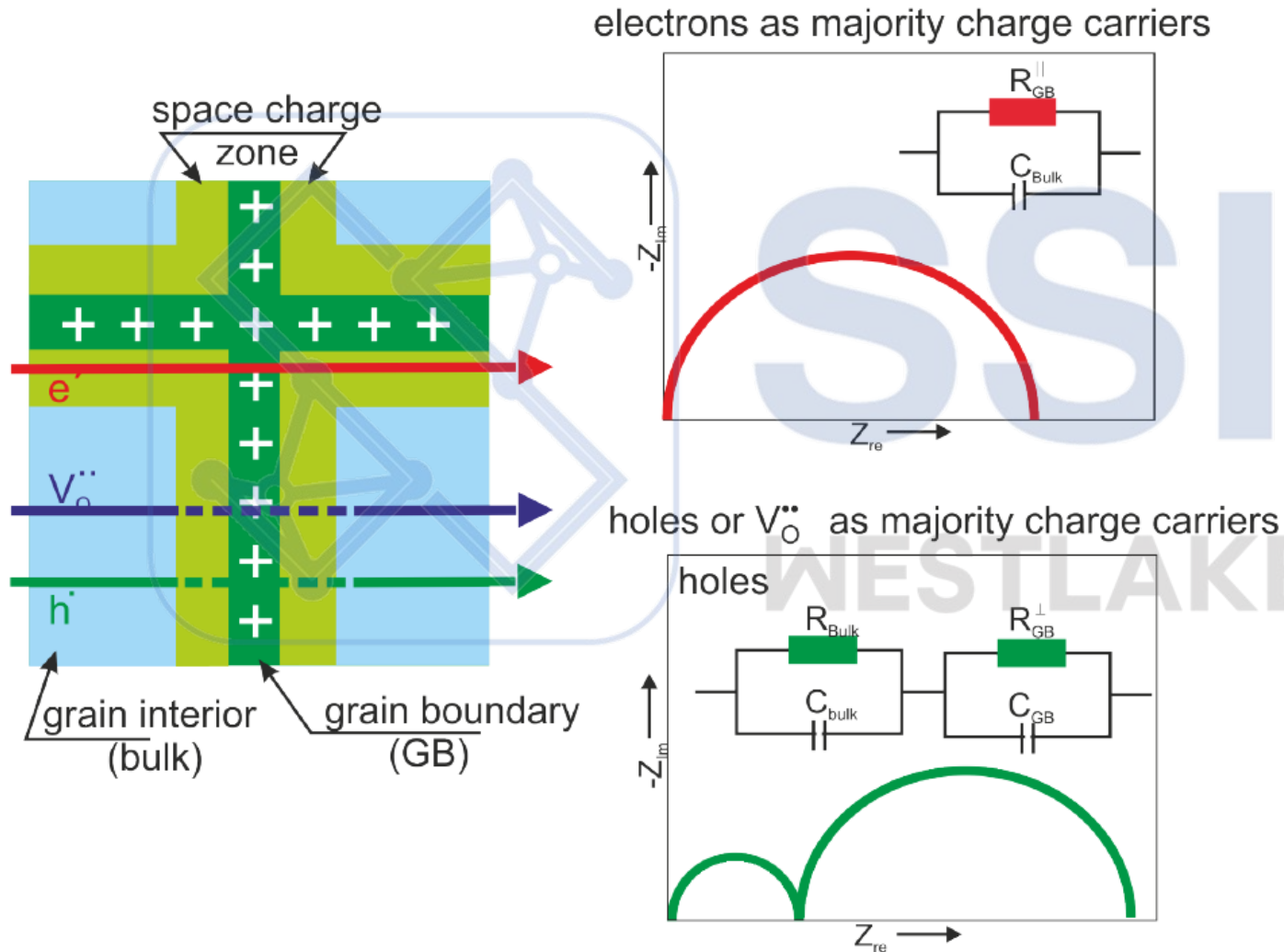Series layer model for different charge carriers



$$\frac{R_{bulk}}{R_{GB}} = \frac{\sigma_{GB}}{\sigma_{bulk}} \frac{D}{d}$$

$$(d \ll D)$$

- If $\sigma_{GB} \ll \sigma_{bulk}$, then path (1) (i.e., **series layer model**) will be dominate; \rightarrow this is the case for V_O'' and h'
- If $\sigma_{GB} \gg \sigma_{bulk}$, then path (2) (i.e., **conducting along GBs**) might be activated. \rightarrow this is the case for e'

Electrochemical Impedance Spectroscopy (EIS):

- Why do we need electrochemical impedance spectroscopy? What problem are we trying to solve with this technique?
- How to understand the equivalent circuit model? How does the equivalent circuit model for a polycrystalline sample with grain boundaries look like?

Goal of this lecture: you should be able to answer the questions above now (hopefully) :)

End of Lecture 8 Solid State Ionics Fall 2022

西湖大學

固态离子学课题组网站



课题组微信公众号

